

# Module-IV

## Control of HVDC Link

### Desirable control Features:

i) Controller should not be sensitive to normal variations in voltage & frequency.

$$50\text{Hz} \pm 0.5\text{Hz}$$

Mismatch between generation & demand

$$\Rightarrow \text{if } G > D, f \uparrow$$

$$\text{if } G < D, f \downarrow$$

ii) Control should be fast, reliable and simple to implement

→ converter control

delay angle control


$$(\alpha)$$

OLTC  $X_{mex}$

→ slow in response

iii) There should be continuous operating range from full rectification to full inversion and vice versa.

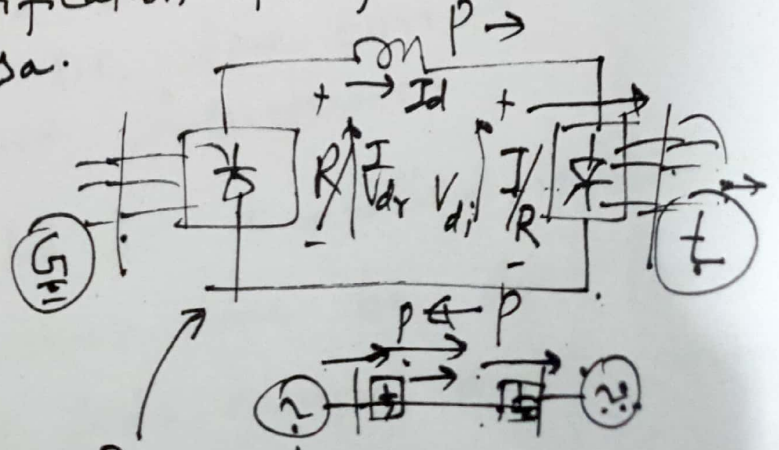iv) Control should be such that it requires less reactive power



Back-to-Back HVDC link


$\alpha$

gf  $\alpha \uparrow$ ,


ca  $\downarrow$ ,

pf  $\downarrow$

$\alpha_{max} \approx 10-25^\circ$

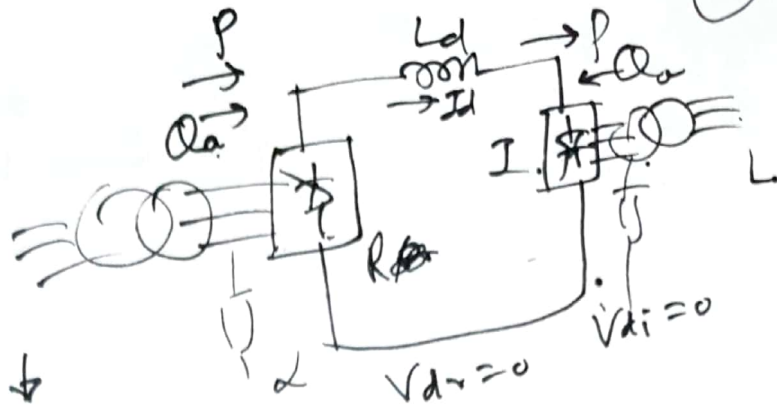

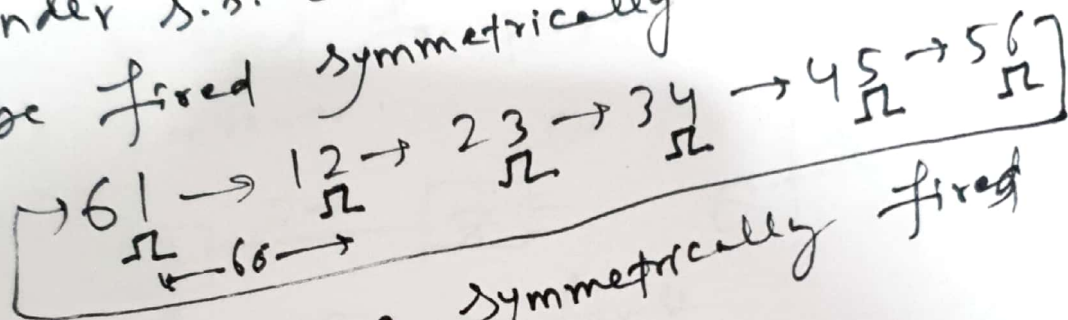v) Under s.s. conditions, the valves must be fired symmetrically



at  $60^\circ$  intervals. Valves are symmetrically fired

Characteristic harmonics,

$$h = np \pm 1$$

5, 7, 11, 13, ...

11, 13, ...

vii) Control should be such that it controls the max. DC line current and limits the current fluctuation.


viii) Power should be controlled independently and smoothly which can be done by controlling the DC side current and/or voltage simultaneously in the line.

$$P_d = V_d \times I_d$$

$V_d \leftarrow \phi$   $I_d$  : constant

$$P_d = V_d \times I_d$$

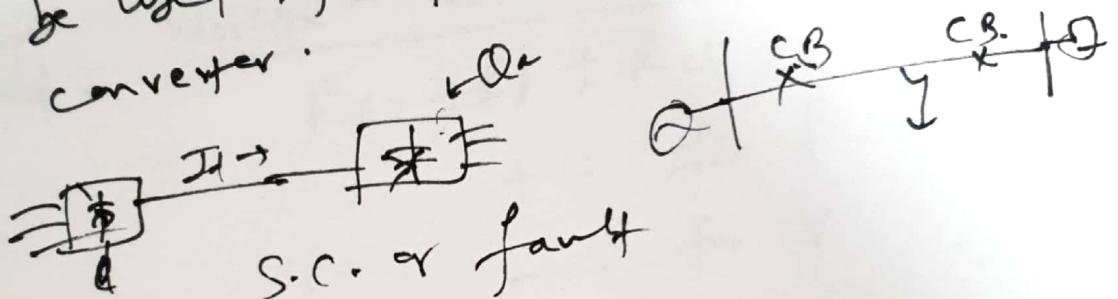Viii) Control should be such that it can be used for protection of line and converter.




S.C. or fault

Control


$$V_{dr} = V_{di} = 0$$

$$I_d = 0 \downarrow$$

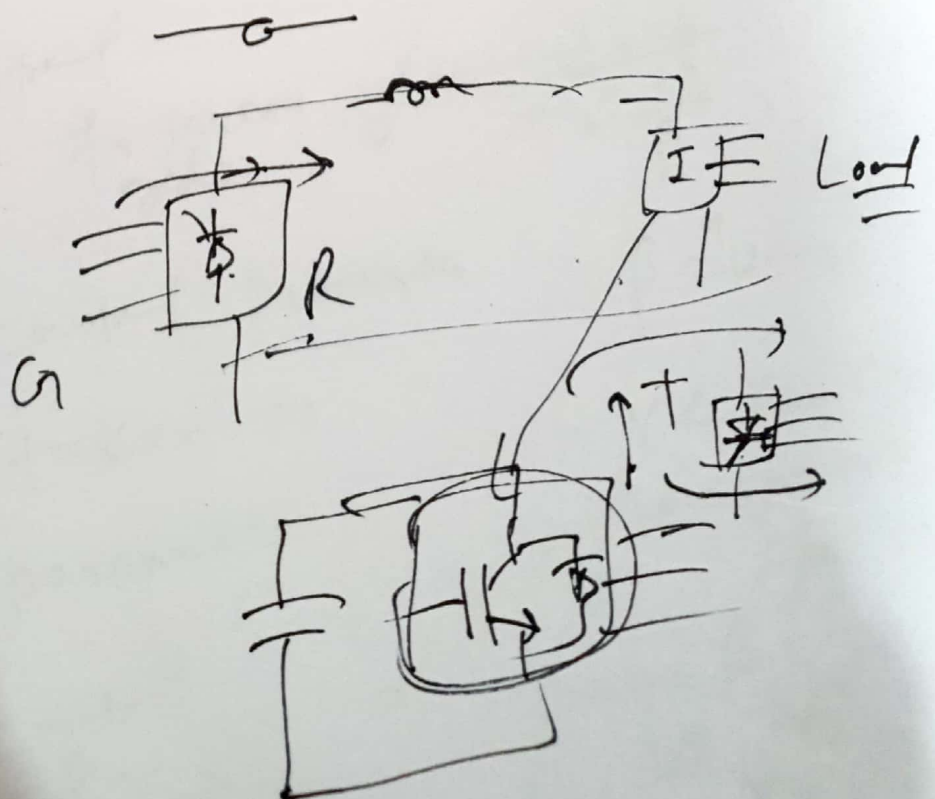

# Control characteristics:

Introduction:

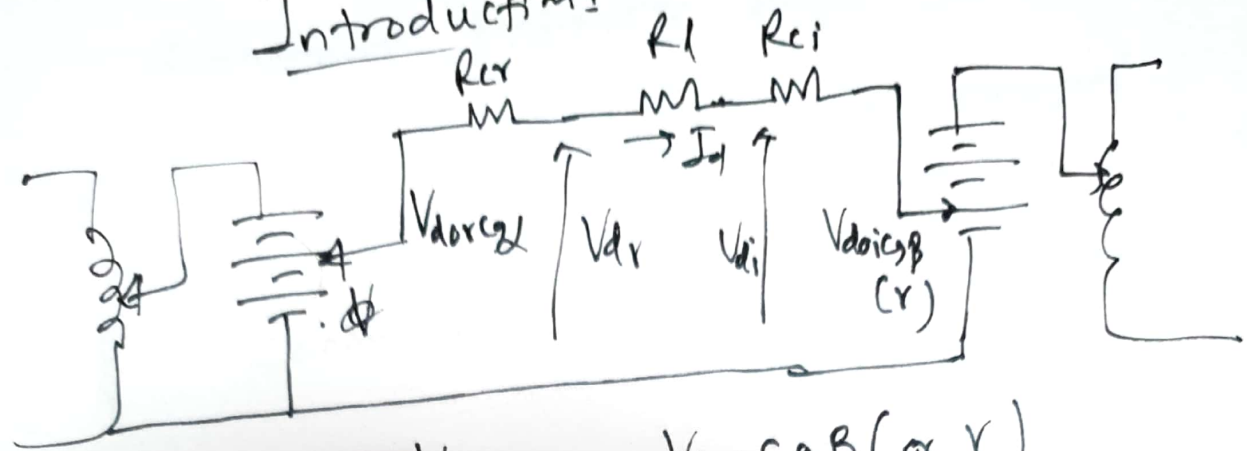


$$I_d = \frac{V_{dorc\gamma} - V_{doiC\gamma\beta} \text{ (or } \gamma)}{R_{cr} + R_l + R_{ci}}$$

+ : for  $\beta$   
 - : for  $\gamma$

$$V_{di} = V_{doiC\gamma\beta} + R_{ci} I_d$$

$$V_{di} = V_{doiC\gamma} - R_{ci} I_d$$

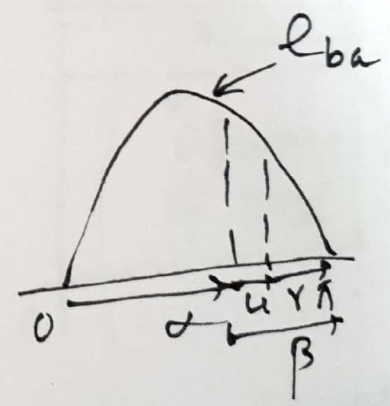-  $\beta$  as control parameter for inverter side



-  $\gamma$  as control parameter

$$\beta = \alpha + \gamma$$

∴  $\gamma$  is taken as control parameter

- $\gamma < \gamma_{min}$  (0 →)
- Commutation failure

$\gamma \rightarrow$  control

$$\gamma \neq \gamma_{min}$$

$$\gamma \geq \gamma_{min}$$

Increase  $\beta$

$$\uparrow \gamma \rightarrow \uparrow V_{di}$$

$$\gamma \geq \gamma_{min}$$

On inverter side, we have  
 Constant Extinction Angle (CEA) control.



$$CEA \rightarrow \gamma = \text{constant at } \gamma_{min.}$$

R: constant Ignition Angle (CIA) control  
 $\alpha \leq \alpha_{max.}$

I: constant Extinction Angle (CEA) control  
 $\gamma = \gamma_{max.} (\text{constant})$

$$V_{dr} = V_{dor} \cos \alpha - (R_r + L_r \frac{di}{dt}) I_d$$
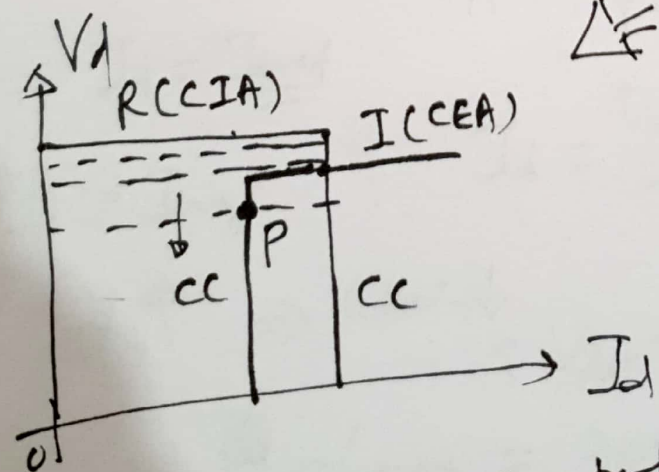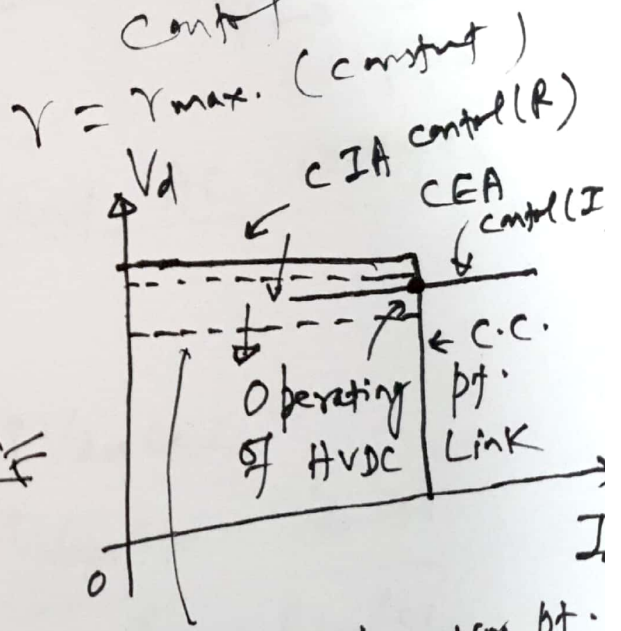
$$V_{di} = V_{doi} \cos \gamma - R_e i I_d$$



No operating pt.  
 → No power transfer


HVDC Link control charact:

$$R: CIA + CC$$

$$I: CEA + CC$$

Effect of AC side voltage on DC link current.

Aim: To keep  $I_d$  always constant.

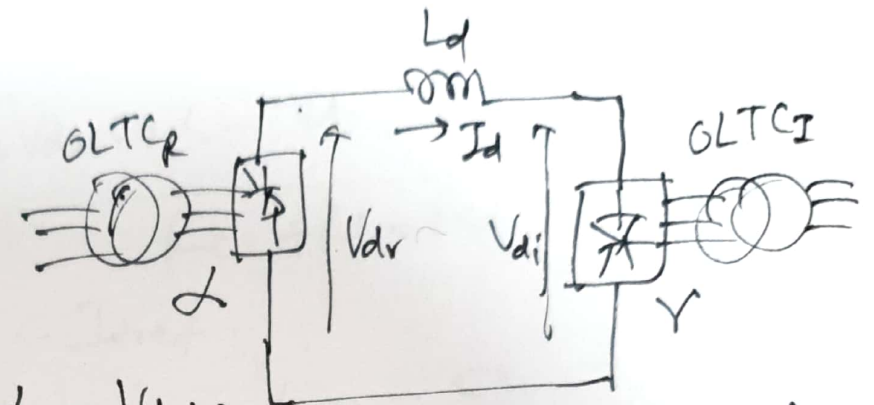

$$I_d = \frac{V_{dor} C_{g\alpha} - V_{doi} C_{g\gamma}}{R_{cr} + R_l - R_{ci}}$$

$\gamma \rightarrow$  comp para

i) Increase in Rectifier-end AC voltage.

$$\uparrow V_{dor} = \frac{3\sqrt{3} E_m}{\pi}$$

Aim:  $I_d = I_{dref}$

$$I_d > I_{dref}$$

$$I_d = \frac{\uparrow V_{dor} C_{g\alpha} - V_{doi} C_{g\gamma}}{R_{cr} + R_l - R_{ci}}$$

$$\alpha \uparrow \Rightarrow C_{g\alpha} \downarrow$$

$$\alpha_{max} = 20 - 25^\circ$$

OLTC\_I

$V_{doi}$

OLTC\_R

$I_d > I_{dref}$

operation  $\rightarrow E_m \downarrow$

$V_{dor}$

$$\Rightarrow \boxed{I_d = I_{dref}}$$

ii) Decrease in Rectifier - end AC voltage:

$$\downarrow V_{dor} = \frac{3\sqrt{3}E_m \downarrow}{\pi}$$

$$\downarrow I_d = \frac{\downarrow V_{dor} C_{gd} - V_{dor} C_{gY}}{R_{cr} + R_l - R_{cr}}$$

$$I_d < I_{dref}$$

$$\alpha_{min} = 5^\circ$$

Controller:

$$\alpha \downarrow$$

$$C_{gd} \uparrow$$

$$I_d < I_{dref}$$

- OLTCR

$$E_m \uparrow$$

$$V_{dor} \uparrow$$

$$I_d < I_{dref}$$

- OLTCI

$$V_{doi} \downarrow$$

$$V_{di} \downarrow$$

$$I_d = I_{dref}$$

iii) Increase in Inverter - side AC voltage:

$$- I_d < I_{dref}$$

CEA

$$V \downarrow$$

$$V_{min}$$

$$R: \alpha \downarrow \quad V_{dor} C_{gd} \uparrow$$

$$I_d < I_{dref} \quad I_d \uparrow$$

$$\alpha_{max} = 5^\circ$$

OLTCR:  $V_{dor}$

$$I_d < I_{dref}$$

OLTCI:  $V_{doi}$

$$I_d = I_{dref}$$

iv) Decrease in Inverter-side AC voltage:

$$\downarrow V_{doi} = \frac{3\sqrt{3}E_m}{\pi}$$

$$I_d = \frac{V_{dor} C_g \alpha - V_{doi} C_g \gamma}{R_{er} + R_l - R_c}$$

$$I_d > I_{ref}$$

$$R = \alpha \uparrow$$

$$C_g \alpha \downarrow$$

$$V_{dor} C_g \alpha \downarrow$$

$$I_d \downarrow$$

$$I_{max} = 2e^{-25^\circ}$$

$$I_d > I_{ref}$$

OLTCR:  $V_{dor} \downarrow$

$$I_d < I_{ref}$$

$$OLTCI: V_{doi} \uparrow$$

$$V_{doi} C_g \gamma \uparrow$$

$$I_d \downarrow$$

$$I_d = I_{ref}$$