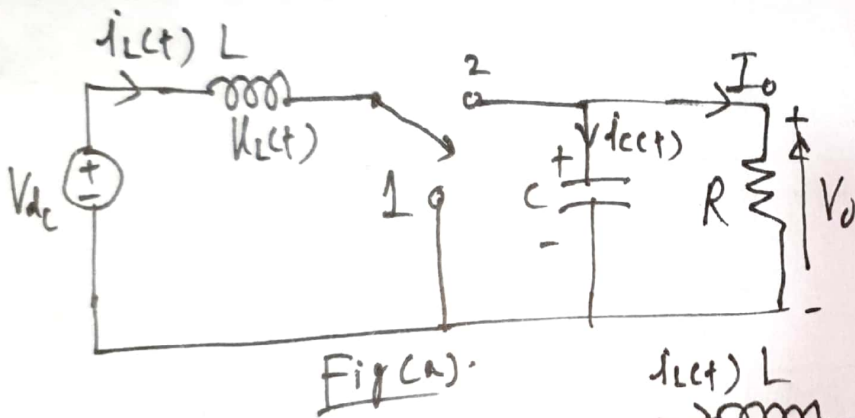



DC-DC Boost Converter / Step-up Chopper:- ①

Its main application is in regulated DC power supplies and regenerative braking of DC motors. As the name implies, the o/p voltage is always greater than the i/p voltage.

Fig. (a) shows the realization of a Boost converter using an SPDT switch and Fig. (b) shows the practical realization of Boost converter, replacing SPDT switch by a power semiconducting device, S and diode, D.



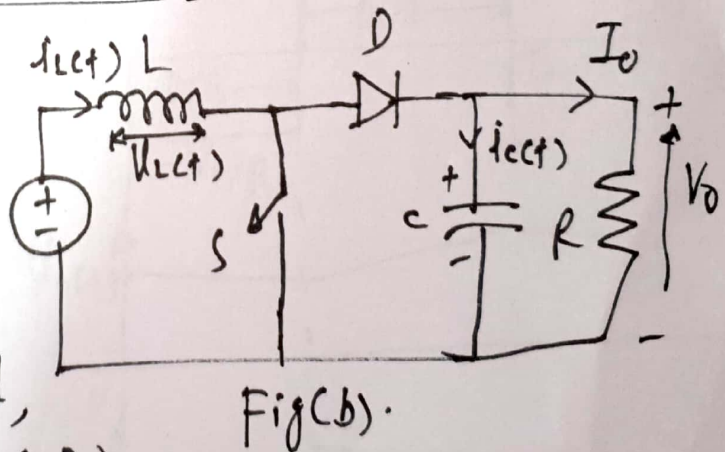During sub-interval, 1 (Energy storage interval), with switch in position 1,




~~$V_L = V_{dc}$~~ (w.r.t. fig (a))


or with S ON (w.r.t. fig (b)), $V_L = V_{dc}$ ①

$$i_C = -V_o / R \quad \text{---} \quad \text{②}$$

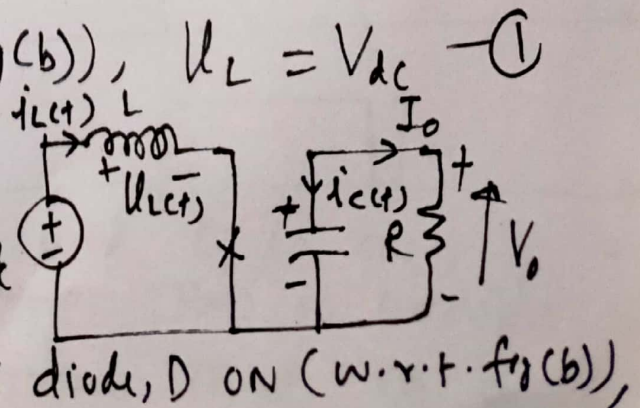During sub-interval 2 (Energy transfer interval), with switch in position, 2 (w.r.t. fig (a)) or diode, D ON (w.r.t. fig (b)),



$$V_L = V_{dc} - V_o \quad (3)$$

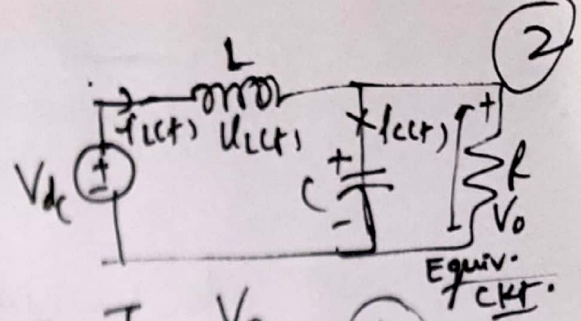


$$i_c = i_L - i_o = i_L - \frac{V_o}{R} = I - \frac{V_o}{R} \quad (4)$$

Above eqns. (1) to (4) are used to sketch the waveforms as below:

During energy storage interval (S ON), $V_L(t)$ is equal to V_{dc} and positive volt-seconds are applied to inductor.

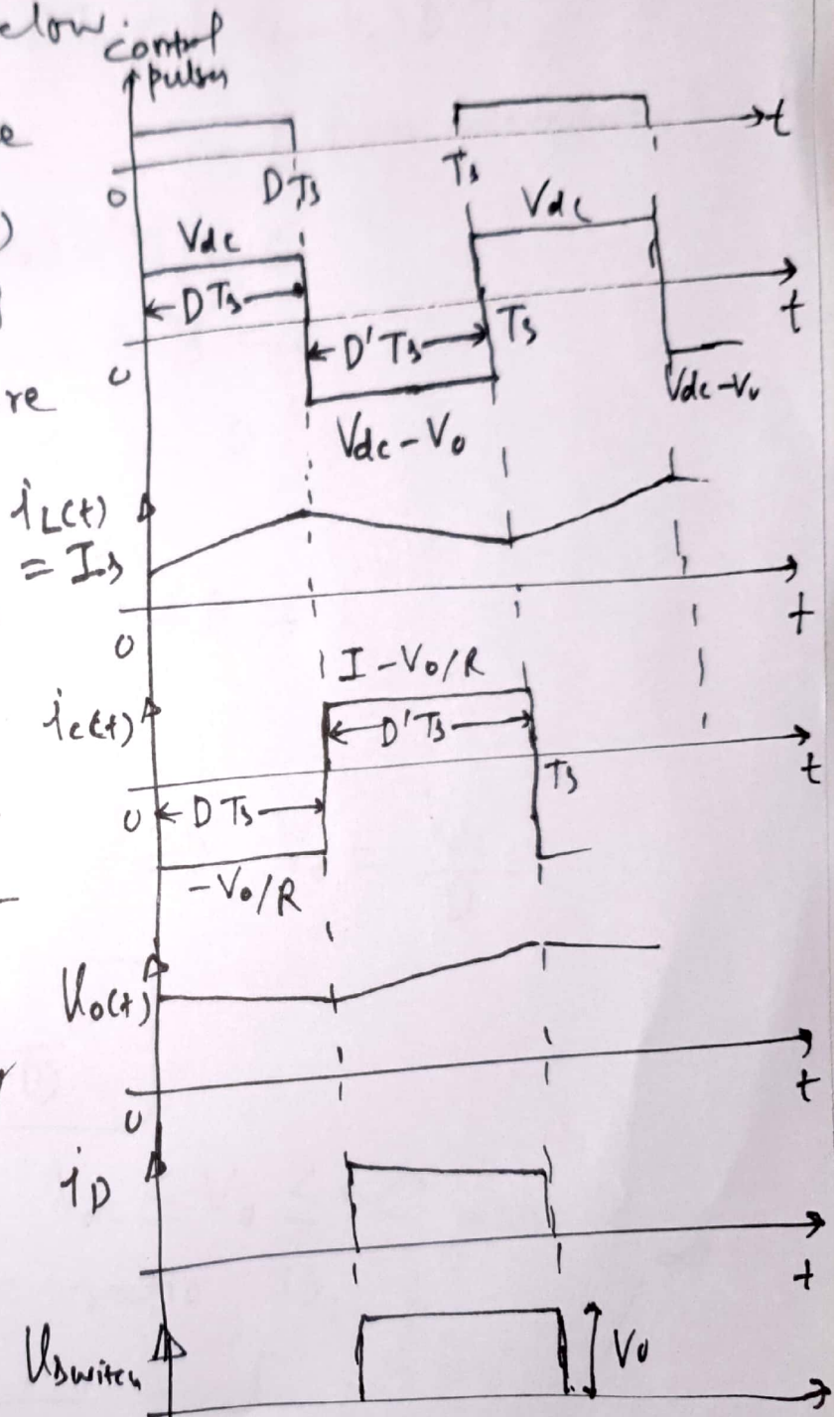Since in steady-state, the total volt-seconds applied over one switching period must be zero, negative volt-seconds must be applied during energy transfer interval (S OFF and D ON), which implies that inductor-voltage during second



sub-interval (when S is OFF and D is ON) i.e., $V_{dc} - V_o$ must be negative. This is possible only if $V_o > V_{dc}$. Hence it proves that in a

boost converter, o/p voltage is always greater than i/p voltage.

Now, total volt-sec. applied to the inductor over one switching period are:

$$\int_0^{T_s} v_L(t) dt = (V_{dc}) \cdot DT_s + (V_{dc} - V_o) D' T_s = 0$$

(from waveforms)

$$\Rightarrow V_{dc} DT_s + (V_{dc} - V_o) D' T_s = 0$$

$$\Rightarrow V_{dc} DT_s + V_{dc} D' T_s - V_o D' T_s = 0$$

$$\Rightarrow V_{dc} (D + D') - V_o D' = 0$$

Since $D' = 1 - D$

$$\therefore D + D' = D + 1 - D = 1$$


$$\therefore V_{dc} - V_o D' = 0$$

$$\Rightarrow V_o D' = V_{dc} \quad \Rightarrow V_o = \frac{V_{dc}}{D'}$$

$$\Rightarrow \boxed{V_o = \frac{V_{dc}}{(1-D)}}$$

For $0 \leq D \leq 1$, $V_{dc} \leq V_o \leq \infty$
 voltage conversion ratio is,

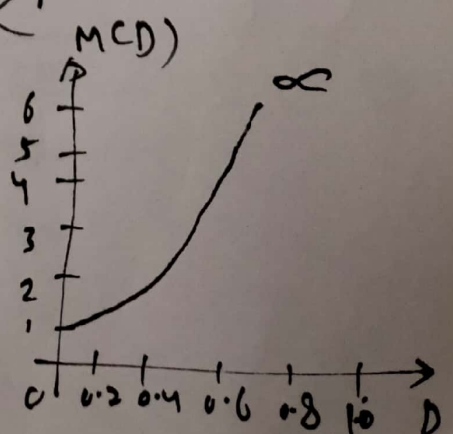
$$M(D) = \frac{V_o}{V_{dc}} = \frac{1}{D'} = \frac{1}{1-D}$$



So, an ideal Boost converter is capable of producing any o/p voltage greater than i/p voltage. There are, of course, limits to the o/p voltage due to component non-idealities.

Let 'r' be the internal resistance of boost inductor, L (Non-ideality).

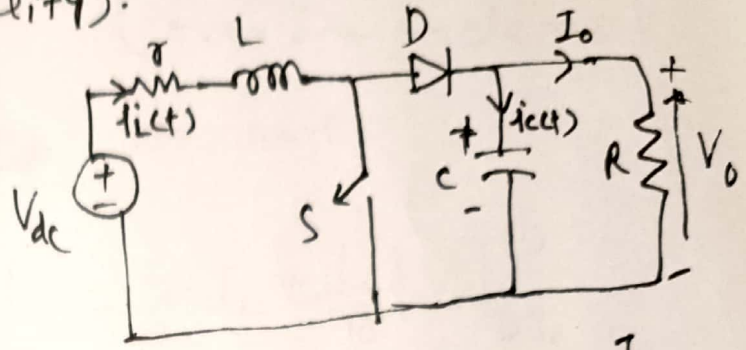Equiv. ckt. during Energy storage interval ($0 < t < DT_s$) is as shown below:




By KVL,

$$V_{dc} = r i_L + L \frac{di_L}{dt} \quad \text{--- (1)}$$

By KCL,
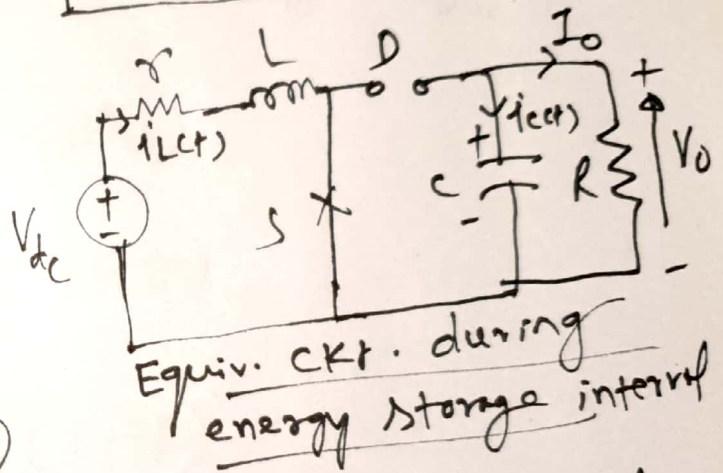
$$C \frac{dv_o}{dt} + \frac{v_o}{R} = 0 \quad \text{--- (2)}$$




Equiv. circuit during Energy transfer interval ($DT_s < t < T_s$) is as:

By KVL,

$$V_{dc} = r i_L + L \frac{di_L}{dt} + V_o \quad \text{--- (3)}$$

By KCL,
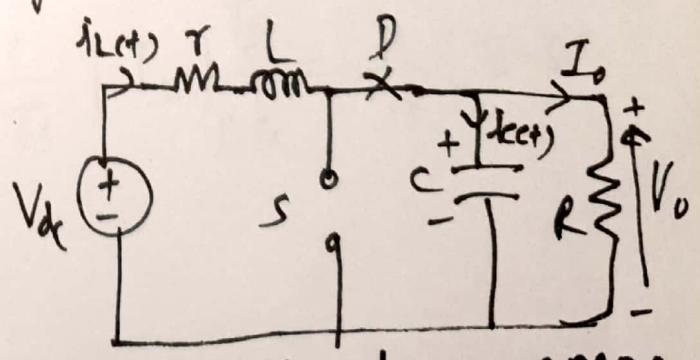
$$C \frac{dv_o}{dt} + \frac{v_o}{R} = i_L \quad \text{--- (4)}$$



Equiv. ckt. during energy transfer interval

Now,

$$V_{dc} = r I_L + L \left(\frac{di_L}{dt} \right) + \frac{1}{T_s} \int_0^{T_s} V_o dt \quad \text{--- (5)}$$

$$C \left(\frac{dv_o}{dt} \right) + \frac{v_o}{R} = \frac{1}{T_s} \int_{DT_s}^{T_s} i_L \cdot dt \quad \text{--- (6)}$$

Now, Average values :

$$V_L = L \int_0^{T_s} \frac{di_L}{dt} dt = 0 \quad (\text{Average inductor voltage over one cycle} = 0)$$

$$I_C = C \int_0^{T_s} \frac{dV_C}{dt} dt = 0 \quad (\text{Average capacitor current over one cycle} = 0)$$

∴ From eqns. (5), ~~and (6)~~ we have

$$V_{dc} = r I_L + \frac{1}{T_s} \int_{DT_s}^{T_s} V_o dt = r \cdot I_L + \frac{1}{T_s} [V_o]_{DT_s}^{T_s}$$

$$V_{dc} = r \cdot I_L + \frac{V_o}{T_s} (T_s - DT_s)$$

$$= r I_L + \frac{V_o}{T_s} \cdot T_s (1-D)$$

$$\Rightarrow V_{dc} = r \cdot I_L + V_o (1-D) \quad \text{--- (7)}$$

From eqn. (6), we have

$$\frac{V_o}{R} = \frac{1}{T_s} \int_{DT_s}^{T_s} i_L dt = \frac{1}{T_s} [I_L]_{DT_s}^{T_s} = \frac{I_L}{T_s} (T_s - DT_s)$$

$$\frac{V_o}{R} = \frac{I_L \cdot T_s}{T_s} (1-D)$$

$$\Rightarrow \frac{V_o}{R} = I_L (1-D) \quad \text{--- (8)}$$

Multiplying eqn. (7) by (1-D), we get

$$V_{dc} (1-D) = r \cdot I_L (1-D) + V_o (1-D)^2$$

Using eqn. (2), we get

$$V_{dc}(1-D) = \gamma \cdot \frac{V_o}{R} + V_o(1-D)^2$$

$$V_o \left[\frac{\gamma}{R} + (1-D)^2 \right] = V_{dc}(1-D)$$

$$\Rightarrow V_o = \frac{V_{dc}(1-D)}{\frac{\gamma}{R} + (1-D)^2}$$

This is the modified expression for average o/p voltage of a practical Boost converter with non-linearities.

For $D=0$, $V_o = \frac{V_{dc}}{\frac{\gamma}{R} + 1} \times R$


For ideal case ($\gamma=0$),

$$V_o = \frac{V_{dc}}{1-D}$$

Question? Why $V_o=0$ for $D=1$ (practically)

and $V_o \neq \infty$ for $D=1$

For $D=1$, equiv. ckt. is as shown

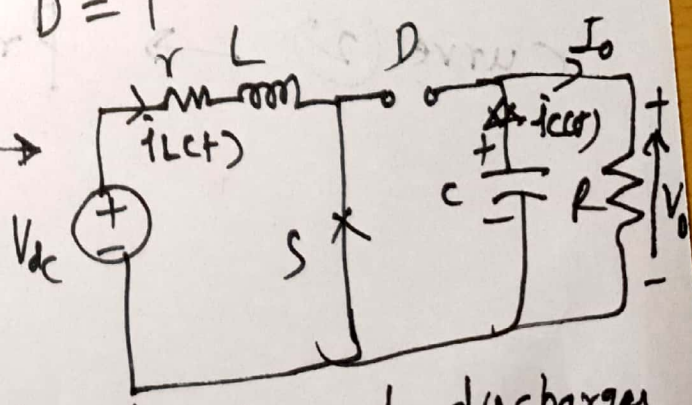

In this case, V_{dc} is predominantly shorted through $L(\gamma)$ and 'C' continuously supplied power to load and discharges.


$$i_C(t) = -I_o = -V_o/R$$

\Rightarrow Capacitor voltage gradually decreases and finally becomes zero (i.e., $V_o = 0$).

On supply side, V_{dc} is applied across L .

So, $L \frac{di_L}{dt}$ is +ive which means inductor current keeps on increasing and we may soon see smoke coming out of the circuit due to the failure or burning of either boost inductor, L or source, V_{dc} or switch, S or all of them as

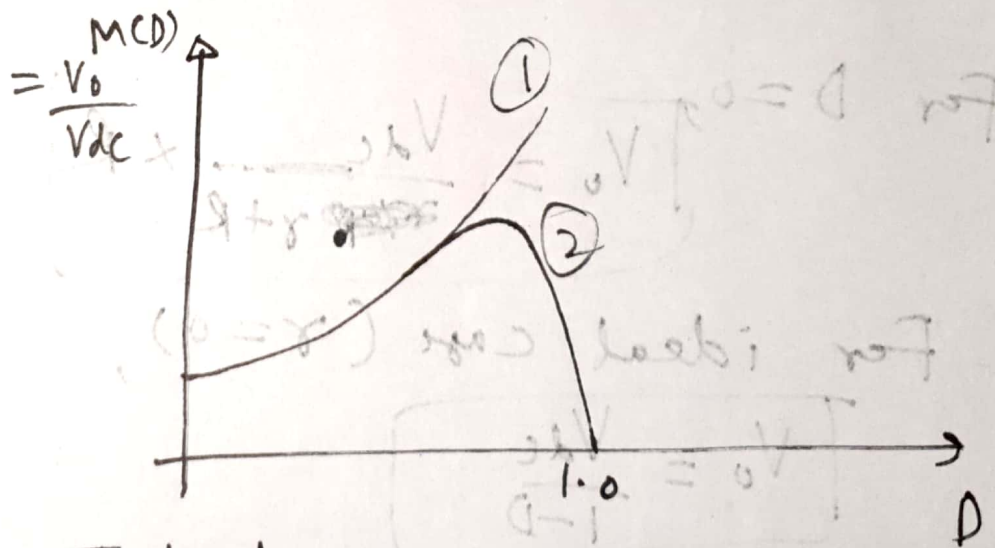$I_{dc} = \frac{V_{dc}}{r}$ is very large.



Curve ① \rightarrow Ideal case

Curve ② \rightarrow Practical case.