



Unit-3

DC-DC converters or Choppers:

DC-DC converters are used in SMPS and in DC motor drives where they are known as choppers, thus, giving chopper-fed DC motor drives.

In all electronic equipment components like transistors and ICs, regulated and reduced-rippled DC biasing voltage is required which is supplied by SMPS. DC-DC converters ~~are~~ in SMPS cause regulated and reduced-rippled DC voltage.

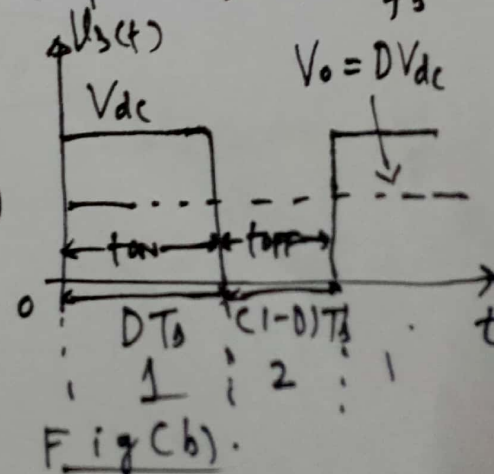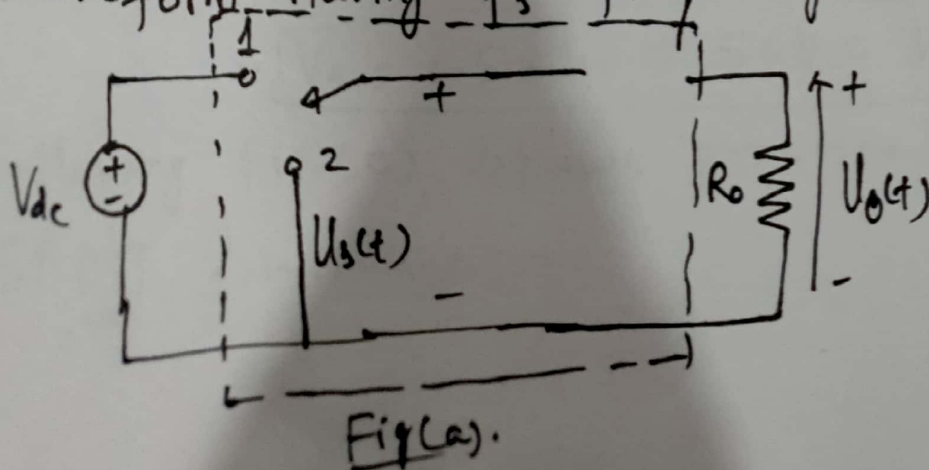Fig(a). Shows the basic working of a DC-DC converter where a Single-Pole-Double-Throw (SPDT) switch is used. The switch o/p voltage is equal to converter i/p voltage when switch is in position, 1 and zero when in position, 2. The switch position is varied periodically as shown in Fig(b) such that $U_s(t)$ is a rectangular waveform having ' f_s ' frequency and period, $T_s = \frac{1}{f_s}$.



The duty ratio, D is defined as the fraction of time in which the switch occupies position, 1. Hence $0 \leq D \leq 1$.

Now, By Fourier series, the DC component of a periodic waveform is its average value.

\therefore Average switch o/p voltage,

$$V_s = \frac{1}{T_s} \int_0^{T_s} u_s(t) dt$$

$$\text{or, } V_s = \frac{1}{T_s} \left\{ \int_0^{t_{on}} u_s(t) dt + \int_{t_{on}}^{T_s} u_s(t) dt \right\}$$

$$V_s = \frac{1}{T_s} \left\{ \int_0^{t_{on}} V_{dc} + 0 \right\} = \frac{V_{dc}}{T_s} \int_0^{t_{on}} dt$$

$$V_s = V_{dc} \cdot \frac{t_{on}}{T_s} = \frac{t_{on}}{t_{on} + t_{off}} \cdot V_{dc}$$

$$\Rightarrow \boxed{V_s = D V_{dc}}$$

$$\therefore 0 \leq D \leq 1 \Rightarrow 0 \leq V_s \leq V_{dc}$$

Let $V_{dc} = 100V$ & $D = 0.5$

$$\therefore \boxed{V_s = 0.5 \times 100 = 50V = V_o}$$

Following Fig. (c) shows practical realization of SPDT Switch.

DC-DC BUCK Converter or Step-down chopper:


(3)

During t_{on} , switch, S is closed and

$$V_s(t) = V_{dc}$$

During t_{off} , S is opened (OFF), the

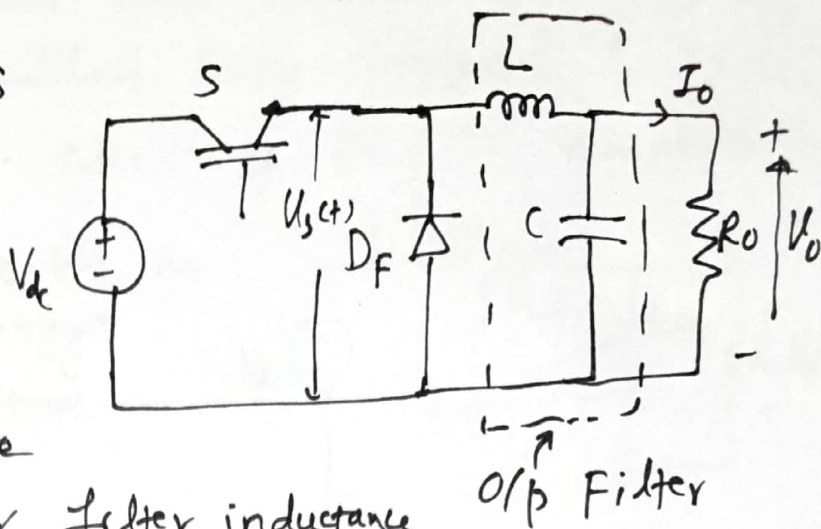energy released by filter inductance freewheels through free-wheeling diode, D_F and load gets shorted through D_F , making load voltage, V_o zero.




\therefore During t_{on} (0 to DT_s period), S is ON & $V_s(t) = V_{dc}$

During t_{off} (DT_s to T_s period), S is OFF & $V_s(t) = 0$.

Now, in addition to desired DC component V_s , the switch o/p voltage, $V_s(t)$ contains undesirable harmonics of switching frequency (due to rectangular nature of $V_s(t)$). To remove the harmonics and make load voltage, $V_o(t)$ essentially equal to DC component, V_s (i.e., $V_o = V_s$), a low-pass L-C filter is connected across load which makes load voltage equal to DC component of switch voltage,

$$\text{i.e., } \boxed{V_o = V_s = DV_{dc}}$$

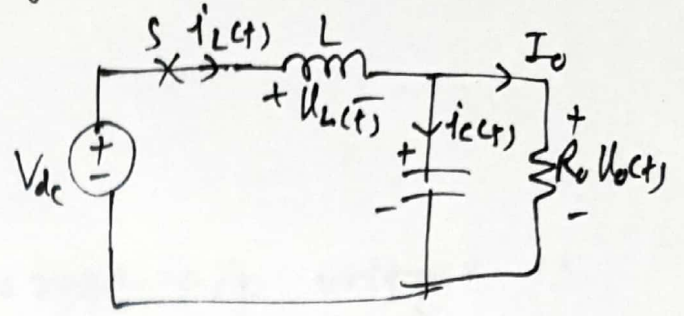Now, During first sub-interval (0 to DT_s), which is also called Duty interval, S is closed and equiv. ckt. of DC-DC converter is,



Inductor current rises as inductor stores energy and inductor voltage ~~During~~ is,


$$v_L = V_{dc} - v_O(t)$$

$$\Rightarrow v_L = V_{dc} - V_o$$


$$v_L = L \frac{di_L(t)}{dt}$$

$$\Rightarrow \frac{di_L(t)}{dt} = \frac{v_L(t)}{L}$$
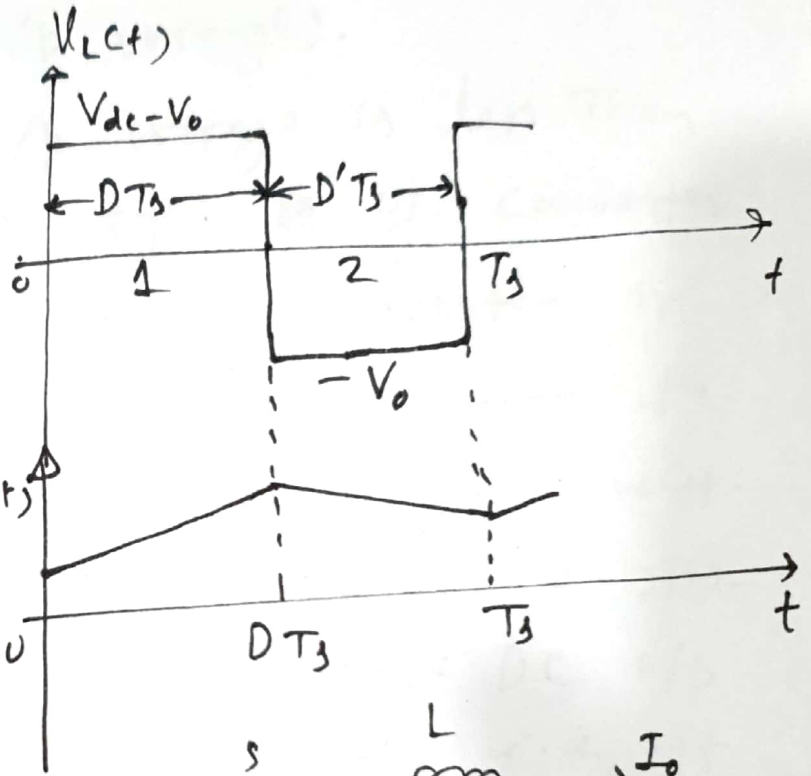
$$\frac{di_o}{dt} = \frac{V_{dc} - V_o}{L} \text{ (+ive slope)}$$



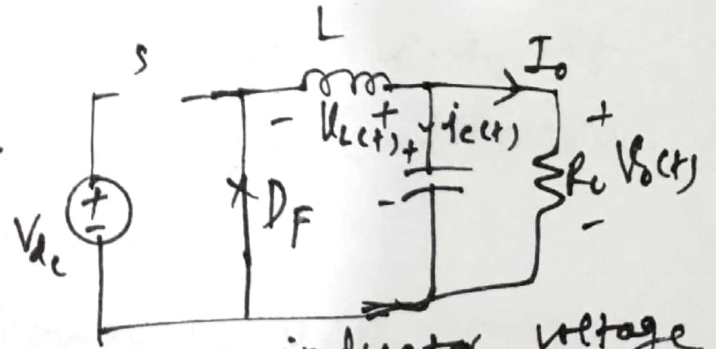During sub-interval, 2 (Freewheeling interval), equiv. ckt. is as shown.



Now, S is OFF & L releases energy and as per volt-sec. balance, the inductor voltage now becomes negative and $i_L(t)$ falls.

$$\therefore v_L(t) = -v_O(t) = -V_o$$

$$\text{As } \frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = -\frac{V_o}{L} \text{ (-ive slope)}$$

Again, DC-DC converter average o/p voltage is,

$$V_o = DV_{dc}$$

As $D < 1$

$V_o < V_{dc}$ (i.e., Average o/p voltage is always less than i/p voltage).



Since average DC o/p voltage is less than DC i/p voltage, this type of converter is called DC-DC Buck converter or Step-down Chopper. It is also equiv. to a ~~transformer~~ step-down transformer of DC circuit. Just like a step-down transformer, a step-down chopper produces an average DC o/p voltage less than DC i/p voltage, i.e., it steps down the DC i/p voltage (although it is not a transformer).

Also, $P_{dc} = P_o$ (i/p power = o/p power for a lossless converter).

$$\Rightarrow V_{dc} \cdot I_{dc} = V_o \cdot I_o$$

$$\Rightarrow \frac{I_o}{I_{dc}} = \frac{V_{dc}}{V_o} = \frac{1}{D}$$

Control Logic:

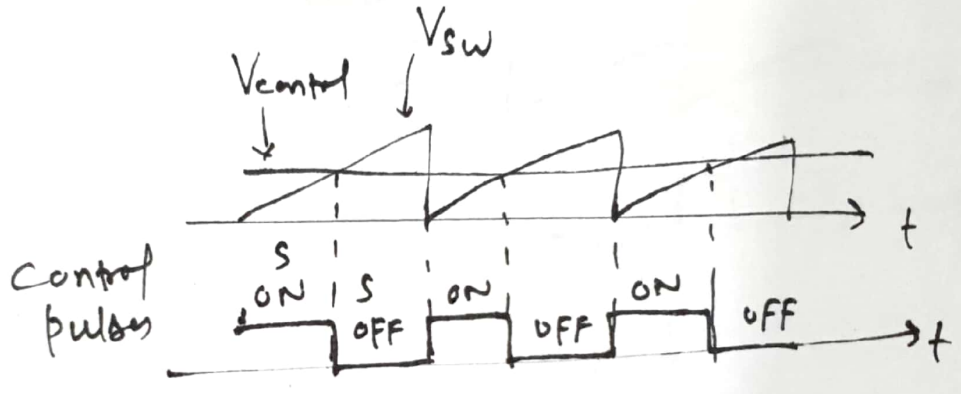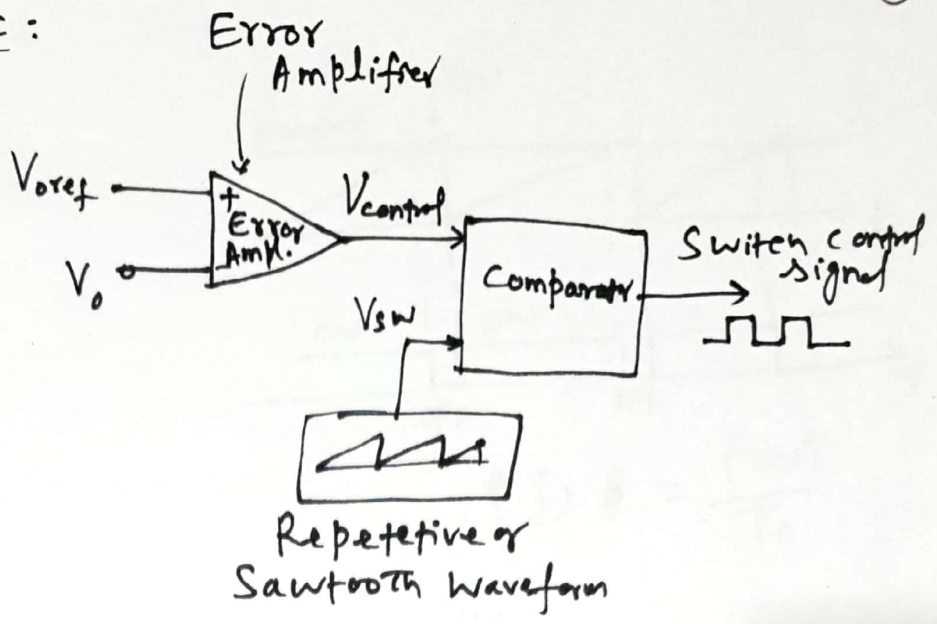



In terms of control signal,

$$D = \frac{t_{on}}{T_s} = \frac{V_{control}}{V_{sw}}$$

$V_{control}$ is a variable control voltage.

As $V_{control}$ increases, ON time of pulse increases & OFF time decreases \Rightarrow D increases and $V_o = DV_{dc}$ also increases.

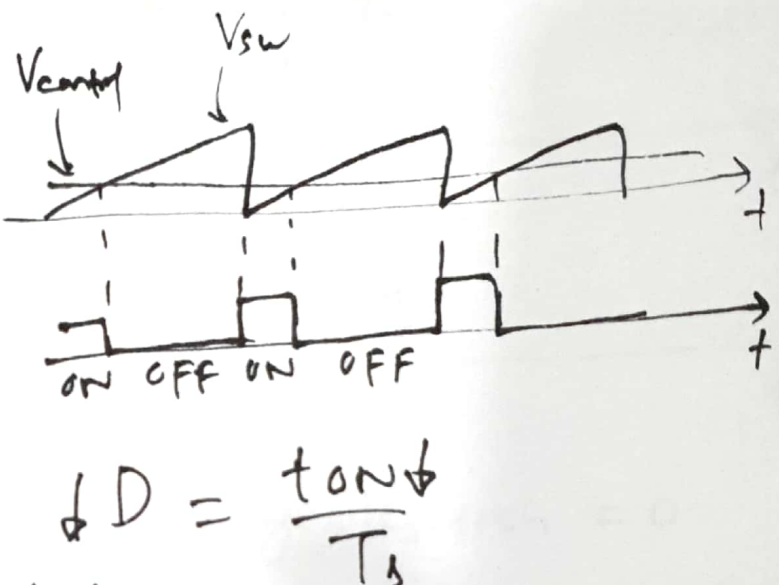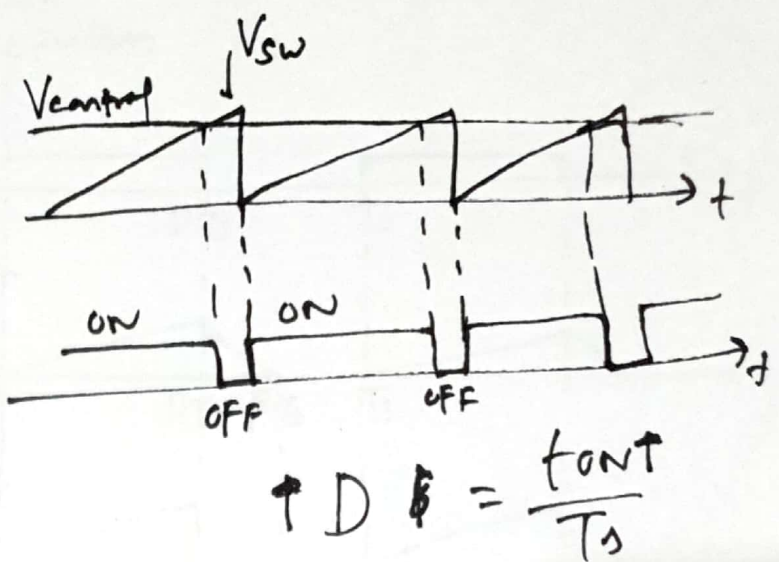As $V_{control}$ decreases, ON time decreases and OFF time increases and D decreases and hence $V_o = DV_{dc}$ decreases.



$V_o = D V_{dc}$ is valid for continuous ~~conduction~~ conduction Mode (CCM), i.e., inductor current, I_L is continuous.


Now, let us consider operation of Buck converter for Discontinuous Conductor Mode (DCM) i.e., when I_L is discontinuous.

Waveforms for DCM are as following:

Equiv. CKT. ~~is~~


for $0 \leq t \leq DT_s$
(0 to DT_s) when

S is ON:

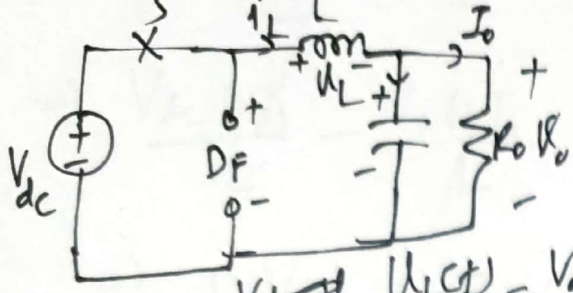

$$\frac{di_L}{dt} = \frac{V_{dc} - V_o}{L} = \frac{V_{dc} - V_o}{L} \quad (+ive)$$

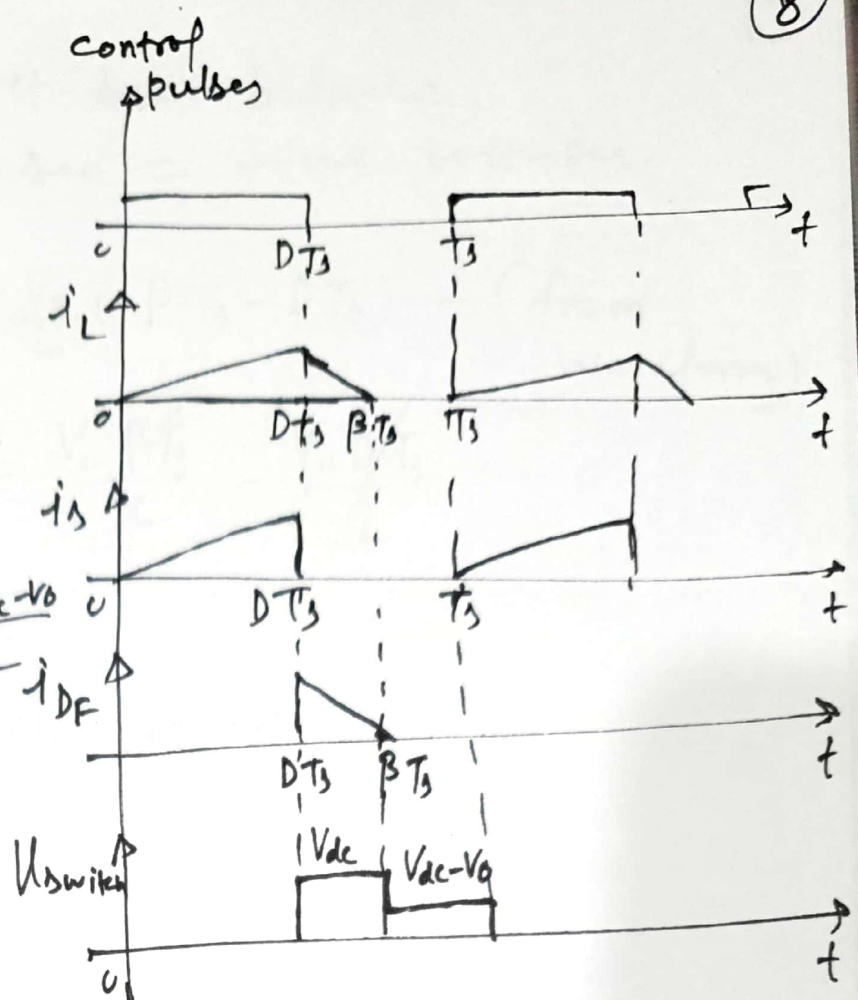
$\Rightarrow i_L$ rises as shown in waveforms. Since 'S' conducts during this period, switch voltage, $V_{switch} = 0$.



Equiv. CKT. during freewheeling interval ($DT_s \leq t \leq \beta T_s$)
i.e., DT_s to βT_s is as:


$$\frac{di_L}{dt} = \frac{V_{LCT}}{L} = \frac{-V_o}{L} \quad (-ive)$$

$\Rightarrow i_L$ falls.

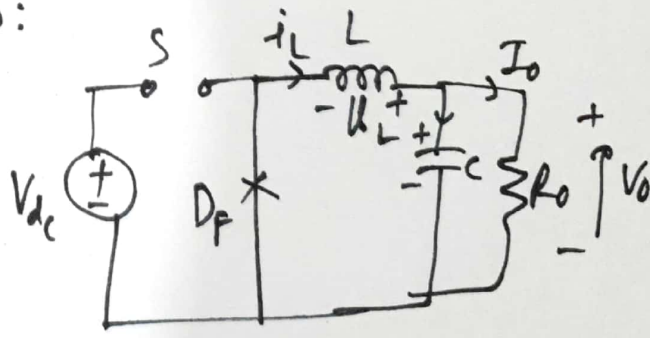

Switch voltage, $V_{switch} = V_{dc}$.
Equiv. CKT. during coasting period ($\beta T_s \leq t \leq T_s$)
i.e., βT_s to T_s is as:

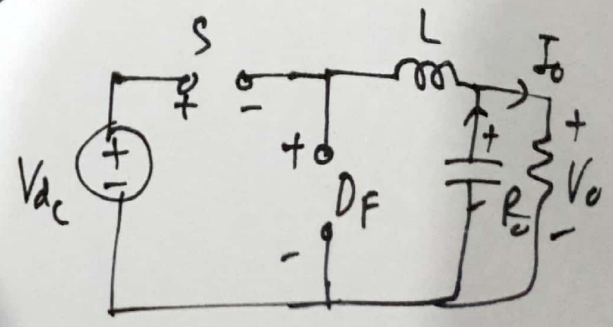Switch voltage,
 $V_{switch} = V_{dc} - V_o$



Now, as per volt-sec. balance,

~~+~~ +ive volt-sec = -ive volt-sec.

$$\Rightarrow \frac{V_{dc} - V_o}{L} \cdot DT_s = \frac{V_o}{L} (\beta T_s - DT_s) \quad \text{--- (from waveform)}$$

$$\Rightarrow \frac{V_{dc} DT_s}{L} - \frac{V_o DT_s}{L} = \frac{V_o \beta T_s}{L} - \frac{V_o DT_s}{L}$$

$$\Rightarrow D V_{dc} = \beta V_o$$

\Rightarrow Average o/p voltage,

$$\boxed{V_o = \frac{D V_{dc}}{\beta}} \quad (\beta < 1)$$

$$\Rightarrow \text{For CCM, } \boxed{V_o = D V_{dc}}$$



$$\text{For DCM, } \boxed{V_o = \frac{D V_{dc}}{\beta}}$$

As $\beta < 1$,


$$V_{oDCM} > V_{oCCM}$$

If load is a DC motor,

for CCM:

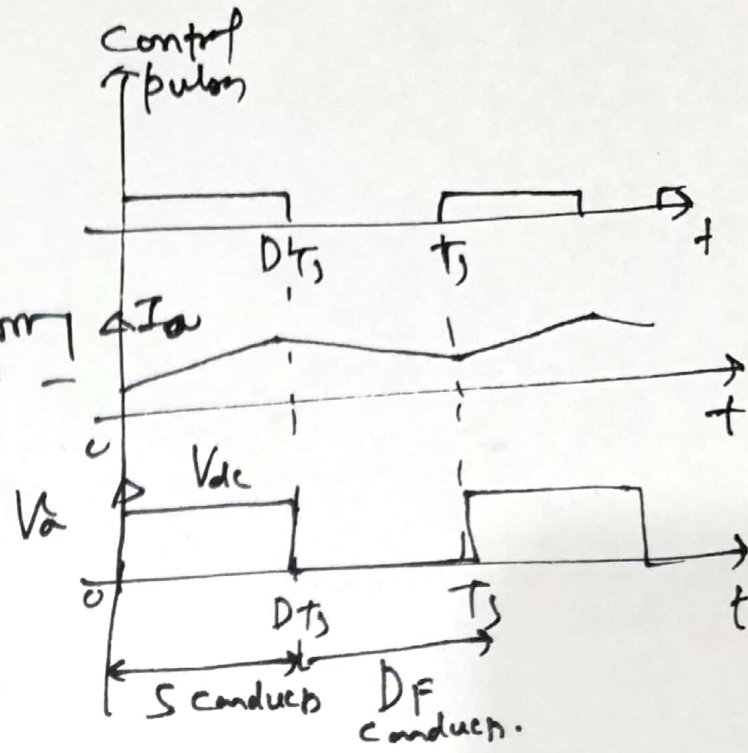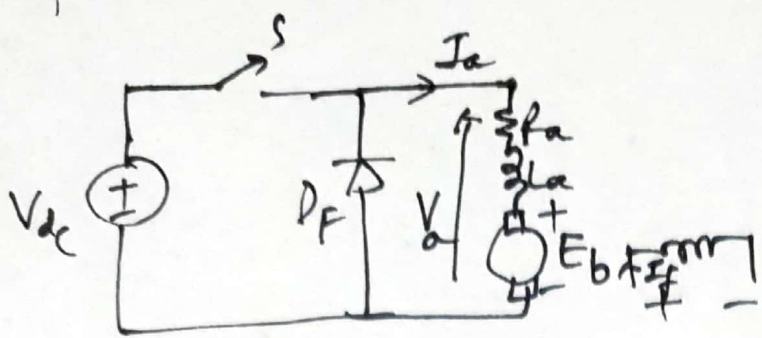

For DCM:

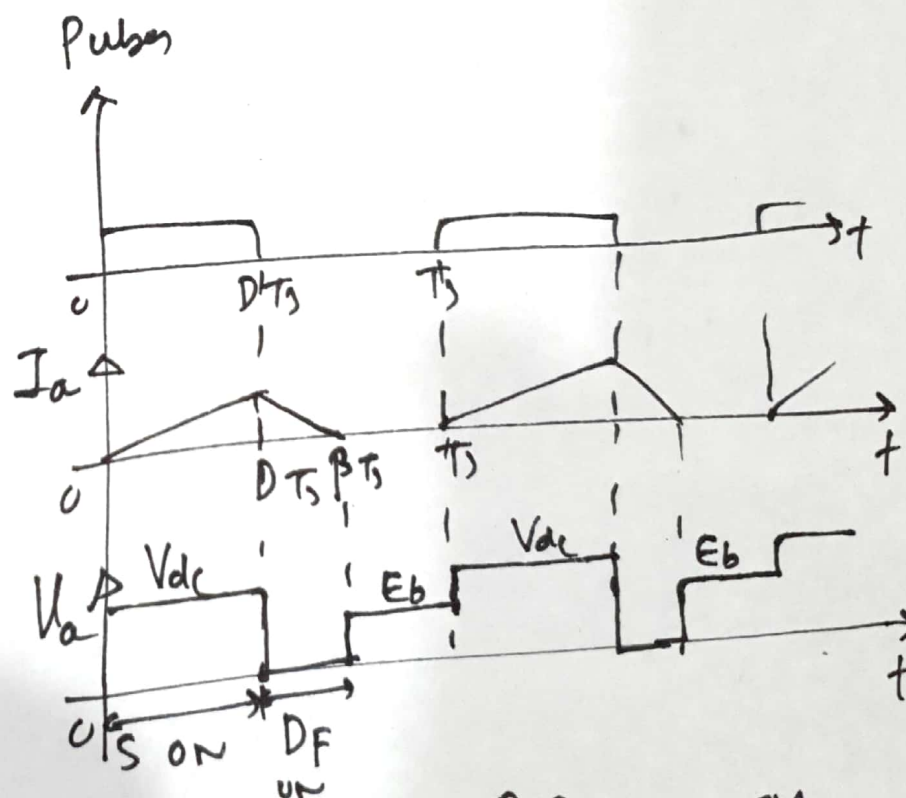

Back Emf, E_b of motor shows its presence in DCM as shown above.