

### ③ Superposition Theorem


The Superposition Principle states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.

The principle of superposition helps us to analyze a linear circuit with more than one independent source by calculating the contribution of each independent source separately.

- I → we consider one independent source at a time while all other independent sources are suppressed. By suppressing a source we mean voltage source is shorted (replaced by 0V) and energy current source is open circuited (replaced by 0I or ∞ resistance).
- II. Dependent sources are kept intact because they are controlled by circuit variables.


#### Example:-

use superposition to find  $v_x$ ;

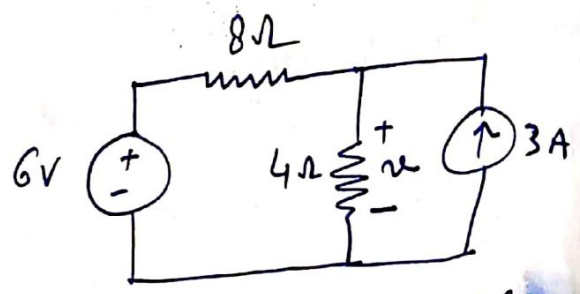

Let the contribution to 'V' due to 6V by  $v_1$  and due to 3A by  $v_2$ ;

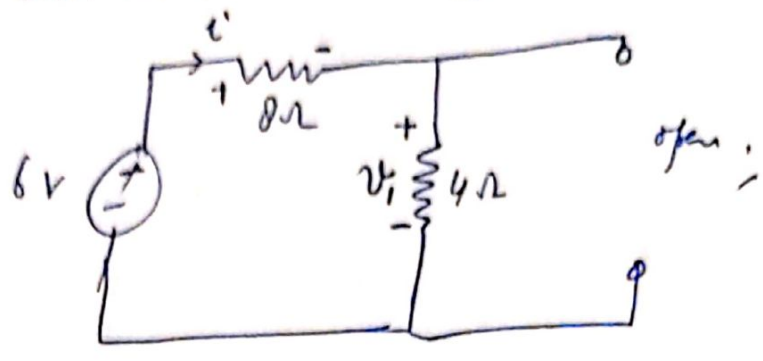
Step I Suppress current source (3A), we are left with.



$$i' = \frac{6}{8+4} = \frac{6}{12} = 0.5 \text{ A}$$

$$V_1 = 0.5 \times 4 = 2.0 \text{ V}$$

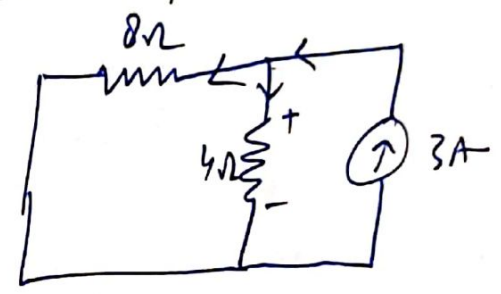Step II: Now suppress 6V and keep (3A) live.



∴ current through 4Ω

$$= 3 \text{ A} \times \frac{8}{8+4}$$
$$= \frac{3 \times 8}{12} = 2 \text{ A}$$


$$\therefore V_2 = 2 \times 4 = 8 \text{ V} \quad \left[ \text{with polarity shown} \right]$$

[ BOTH in same direction ]

$$\therefore V = V_1 + V_2$$

$$V = 2.0 + 8 \text{ V} = 10 \text{ V}$$

Exp.

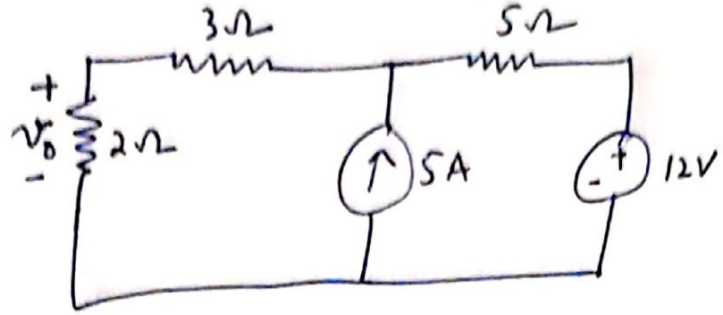


Find  $V_0$  using superposition theorem.

Step I.

Suppress (5A) source & keep 12V source live.

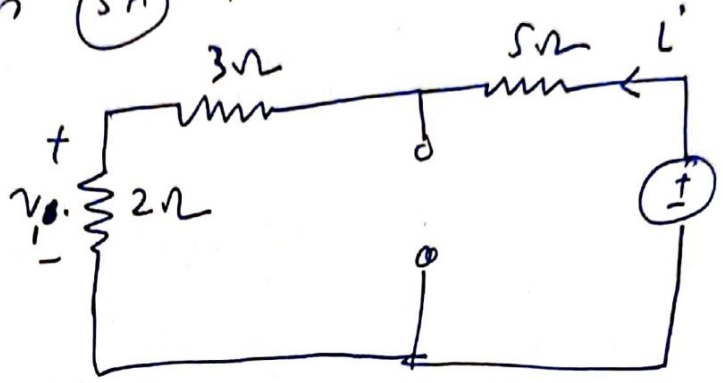
$$I' = \frac{12}{2+3+5} = \frac{12}{10} = 1.2A.$$



$$\therefore V_1 = 1.2 \times 2 = 2.4V \text{ [Polarity shown]};$$


Step II

Keep (5A) live & suppress 12V source.

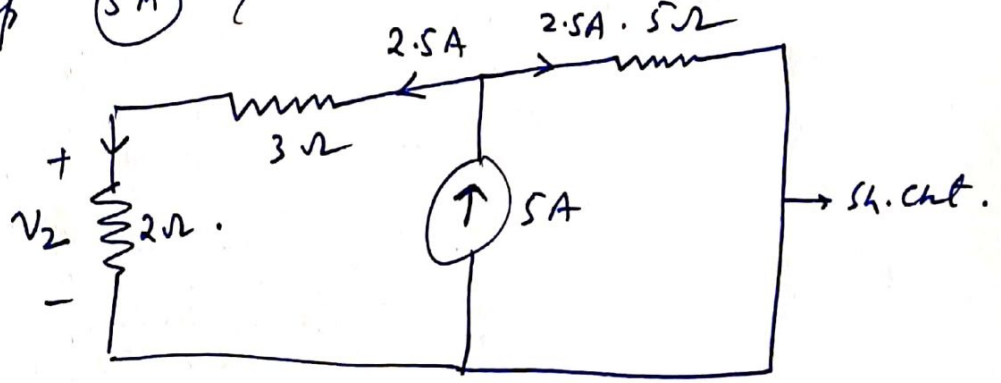


$$V_2 = 2.5 \times 2 = 5.0V \text{ [Polarity + - top to bottom]};$$

$$\therefore V = 2.4 + 5.0 = 7.4V.$$

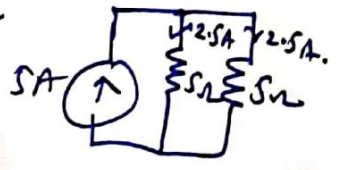

$$\therefore \boxed{V_0 = 7.4V} \checkmark$$

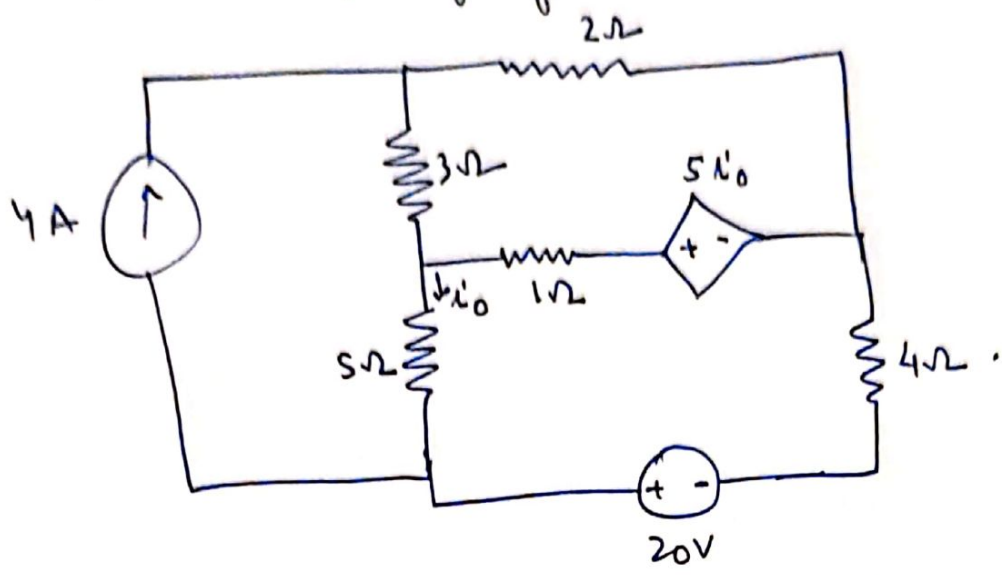Example: Comprising of Both dependant + independent sources.




" Find  $i_o$  using Superposition Theorem "

The dependant source  $5i_o$  has to be left intact.

Let  $i_o = i_o' + i_o''$

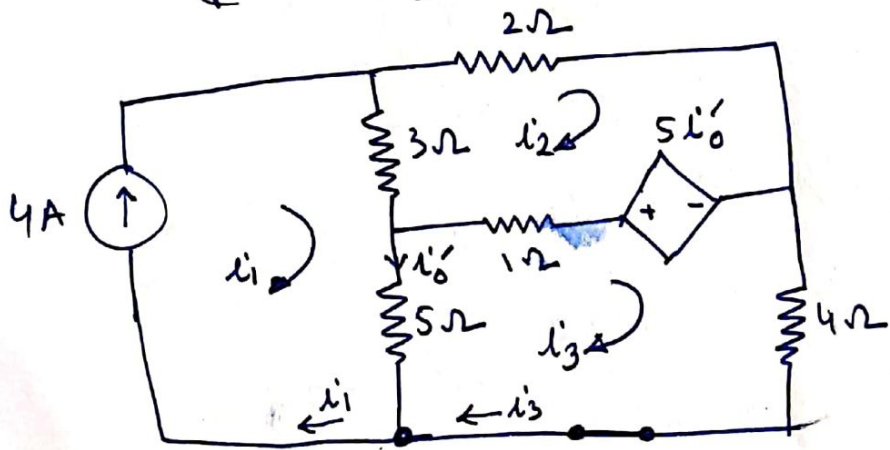where  $i_o' =$  contribution due to  $4A$  current source,  
 $i_o'' =$  " " " "  $20V$  voltage source;



$i_1 = 4A$       ①  $i_1$   
 ~~$5i_o = 5i_2$~~   
 KVL:  $(2+3+1)i_2 - 3i_1 - i_3 = 5i_o$   
 $-3i_1 + 6i_2 - i_3 - 5i_o = 0$       ②

Loop 3.

$$-5i_1 - i_2 + 10i_3 = -5i_0' \quad \text{--- (3)}$$

KCL at node 0;  $i_0' + i_3 = i_1$

$$\therefore i_3 = i_1 - i_0' \quad \text{--- (4)}$$

$$i_3 = 4 - i_0'$$

Substituting =n (1) & (4) in (2) & (3), we get:

$$\text{=n (2):}$$
$$-3i_1 + 6i_2 - (4 - i_0') - 5i_0' = 0$$

$$-5i_1 - i_2 + 10(4 - i_0') + 5i_0' = 0$$

$$-12 + 6i_2 - 4 + i_0' - 5i_0' = 0$$

$$6i_2 - 16 - 4i_0' = 0$$

$$3i_2 - 2i_0' = 8 \quad \text{--- (5)}$$

$$\text{=n (3):}$$
$$-5 \times 4 - i_2 + 10(4 - i_0') + 5i_0' = 0$$

$$-20 - i_2 + 40 - 10i_0' + 5i_0' = 0$$

$$-i_2 + 20 - 5i_0' = 0$$

$$i_2 + 5i_0' = 20 \quad \text{--- (6)}$$

Solve (5) & (6); to get  $i_0' = ?$

from (6)  $i_2 = 20 - 5i_0'$

from (5);  $3(20 - 5i_0') - 2i_0' = 8$


$$60 - 15i_0' - 2i_0' = 8$$

$$-17i_0' = 8 - 60 = -52$$

$i_0' = \frac{52}{17} \text{ A}$

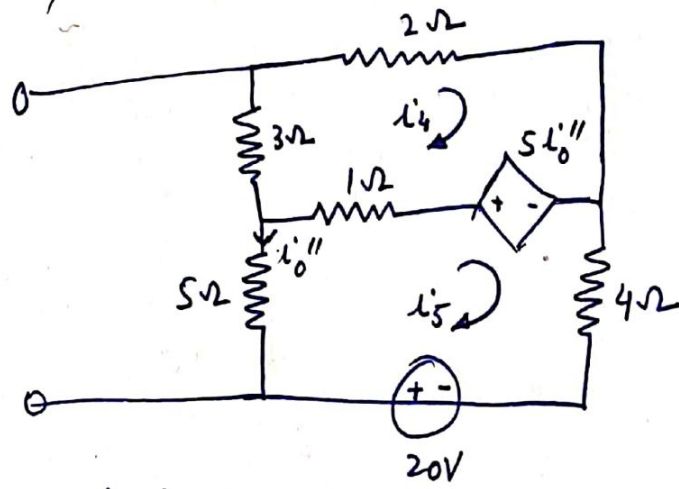(7);

Now Let us suppress the (4A) source and keep 20V source live, we get;



Apply mesh analysis:-

Mesh 4;  $6i_4 - i_5 = 5i_0''$  ————— (8)

Mesh 5;  $-i_4 + 10i_5 = 20 - 5i_0''$  ————— (9)

Also;  $i_5 = -i_0''$  ————— (10);

From eq (8);  $6i_4 - (-i_0'') = 5i_0''$   
 $6i_4 + i_0'' - 5i_0'' = 0$

$$6i_y - 4i_0'' = 0 \quad \text{--- (11)}$$

From (9);

$$-i_y + 10(i_0'') = 20 - 5i_0''$$

$$-i_y = 20 - 5i_0'' + 10i_0''$$

$$-i_y = 20 + 5i_0'' \quad \text{--- (12)}$$

From (11);

$$6(-20 - 5i_0'') - 4i_0'' = 0$$

$$-120 - 30i_0'' - 4i_0'' = 0$$

$$-120 - 34i_0'' = 0$$


$$i_0'' = \frac{-120}{34} = -\frac{60}{17} \text{ A.} \quad \text{--- (13)}$$

$$\therefore i_0'' = i_0' + i_0''$$

$$= \frac{52}{17} - \frac{60}{17}$$

$$i_0 = \frac{52 - 60}{17} = \frac{-8}{17} = -0.4706 \text{ A.}$$

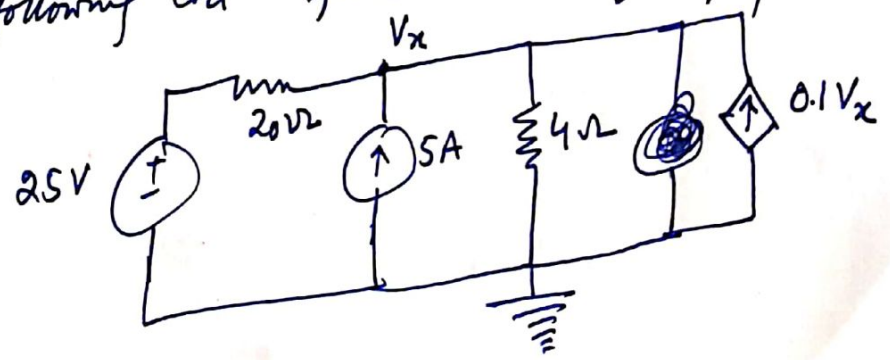Expt. For the following ckt find  $V_x$  using superposition principle.



$$V_x = 31.25 \text{ V}$$